



EEC2146: Electronic Circuits and Measurements

Prepared by:
Dr. Hossam Kasem

Email:
hossam.kasem@f-eng.tanta.eg
hossamkasem1@gmail.com



EEC2146: Electronic Circuits and Measurements



schedule of Classes

- **Lectures:**
 - Wednesday 8:30 pm to 11:30 in Room 11.
- **Instructor office hours every Tuesday from 12:30 pm to 1:30 p.m.**



EEC2146: Electronic Circuits and Measurements



Tutorials

- Every week the instructor will assign a problem set from the text book that deals with the covered sections in the lectures.
- In the tutorial, some of the assigned problems will be worked out on the board.
- At the end of some tutorials you will be asked to solve and submit one or two of the assigned problems. (At least three quizzes will be conducted during this course).
- At the beginning of the following week you will be asked to hand in another set of problems (assignment).



EEC2146: Electronic Circuits and Measurements

Marking Scheme

Quizzes (2 Quizzes)	10 Degrees
Assignments	5 Degrees
Attendance	5 Degrees
Mid Term	15 Degrees
Lecture Activity	5 Degrees
Final	85 Degrees
Total	125

Final Exam Time : 3 Hours



EEC2146: Electronic Circuits and Measurements



Course Objectives

- Analyze the performance of the amplifier circuits response under different frequencies.
- Analyze the performance of practical Power amplifier circuits.
- Identify the different type of feedback and analyze the amplifier circuits under feedback effect.
- Write the equations of voltage gain and input impedance and o/p impedance of different operational amplifier circuits .
- Analyze the power supply circuits.



Course Time Table

Day	Content
30/9/2015	Review over DC and AC Analysis of BJT
7/10/2015	Review over DC and AC Analysis of FET
14/10/2015	LEC.1 On Frequency Response
21/10/2015	LEC.2 On Frequency Response
28/10/2015	LEC.1 On Power Amplifier
4/11/2015	LEC.2 On Power Amplifier
11/11/2015	LEC.1 On Feedback
18/11/2015	Mid Term Exam
25/11/2015	LEC.2 On Feedback
2/12/2015	LEC.1 Op- Amp
9/12/2015	LEC.2 Op- Amp
16/12/2015	LEC.3 Op- Amp
23/12/2015	LEC.1 Power Supply
30/12/2015	LEC.2 Power Supply



BJT Transistors



Objectives and outline:

1. Structure of BJT transistors
2. Basic operation
3. Modes of operation
4. Integrated Circuits NPN and PNP Transistors
5. I-V characteristics of A practical BJT
6. DC analysis
7. Small signal model of BJT
8. AC analysis of BJT Amplifiers



BJT Transistors

1. Structure of BJT transistors

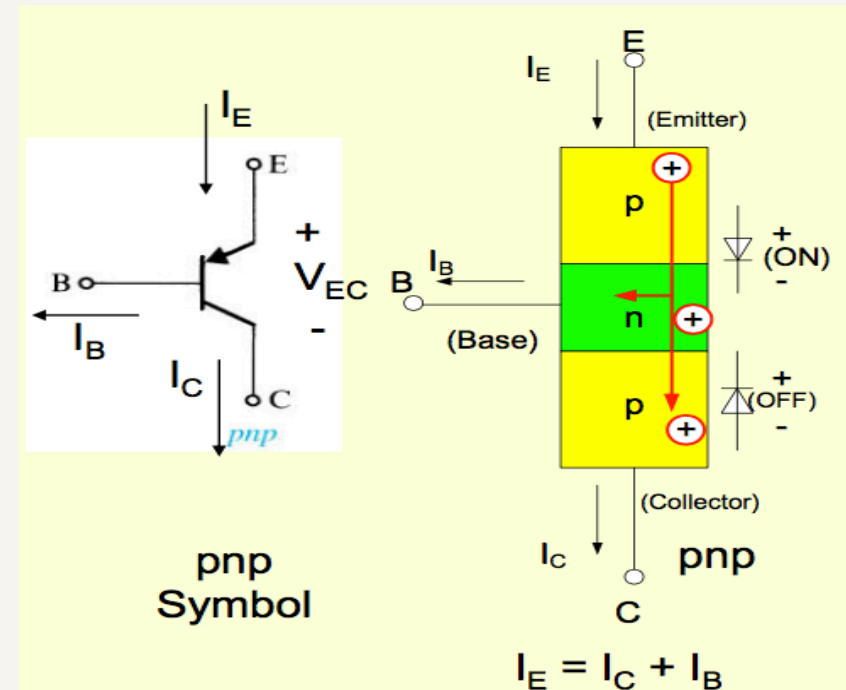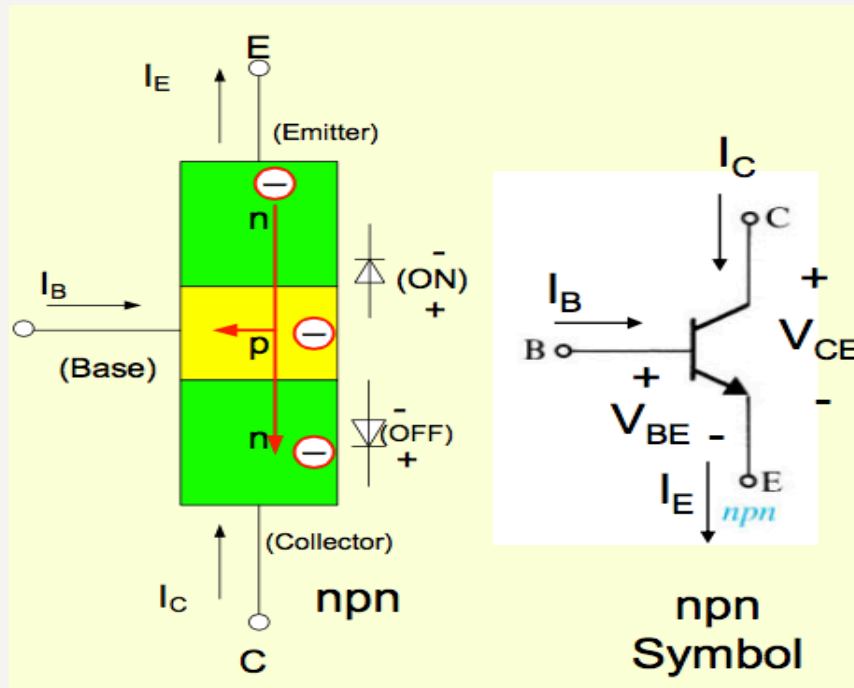



EEC2146: Electronic Circuits and Measurements


BJT Transistors

Modes of Operation

<i>EB Junction</i>	<i>CB Junction</i>	<i>Mode</i>
ON ($V_{BE} = 0.7 \text{ V}$)	Off (O.C)	Active mode (Amplification mode)
ON ($V_{BE,sat} = 0.7$)	ON ($V_{BC,sat} = 0.5$)	Saturation mode (switch)
Off (O.C)	Off (O.C)	Off mode (switch)


BJT Transistors

I-V characteristics of A practical BJT

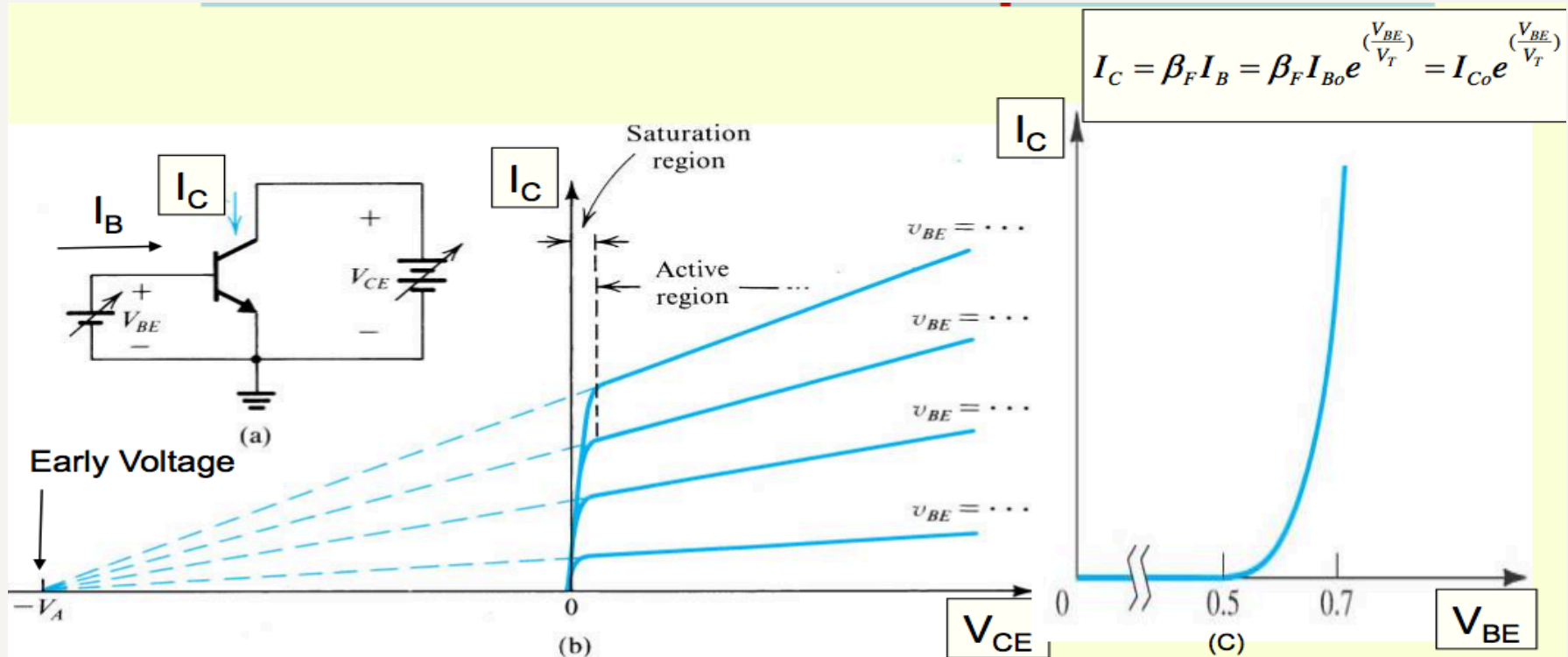

BJT Transistors

I-V characteristics of A practical BJT

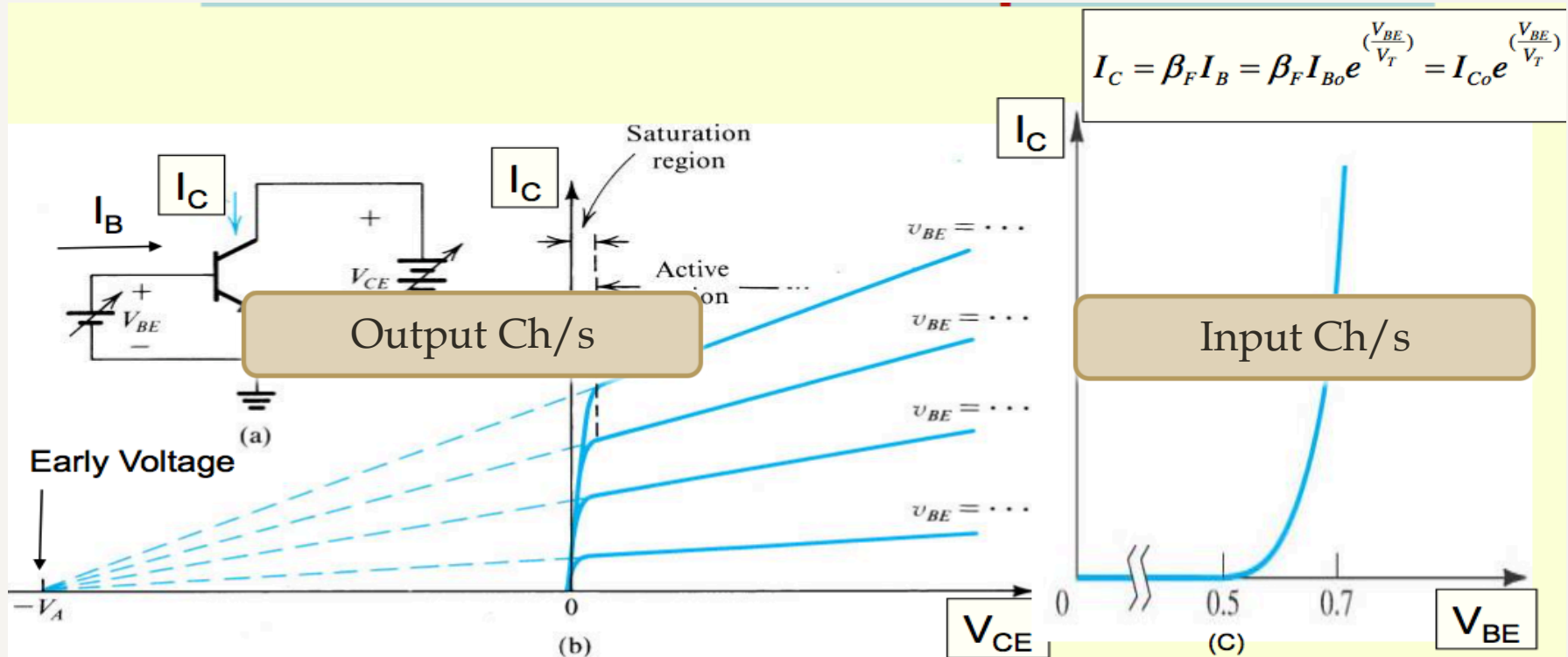



EEC2146: Electronic Circuits and Measurements

BJT Transistors

DC Analysis:

- Determine the type of BJT (i.e. **NPN** or **PNP**).
- Determine the terminals of BJT (**E**, **B**, **C**).
- Distribute the currents on the BJT (**I_E** , **I_C** , **I_B**).
- Distribute different voltage on the BJT (**V_{BE}** , **V_{CE}**).
- KVL around V_{BE} loop.(determine I_B).
- KVL around V_{CE} loop.

$$V_{BE} = 0.7 \text{ V}$$

$$I_E = (\beta + 1)I_B \cong I_C$$

$$I_C = \beta I_B$$



EEC2146: Electronic Circuits and Measurements


BJT Transistors

DC Analysis (Fixed Bias):


$$V_{BE} = 0.7 \text{ V}$$

$$I_E = (\beta + 1)I_B \cong I_C$$

$$I_C = \beta I_B$$

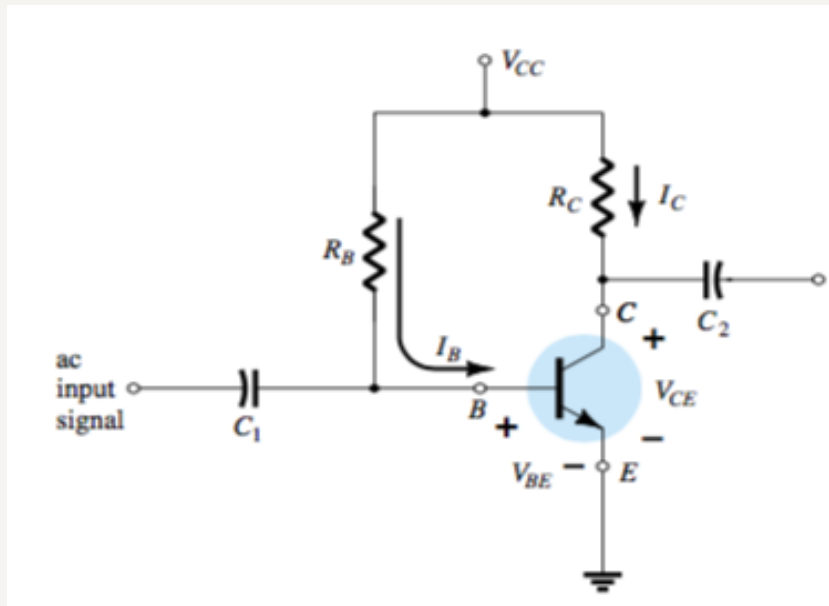

DC Analysis

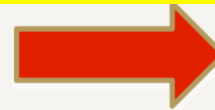

- 1- Put all capacitors O.C.
- 2- Put all coils O.C.
- 3- Put all A.C sources short circuit.



EEC2146: Electronic Circuits and Measurements


BJT Transistors

DC Analysis (Fixed Bias):


$$V_{BE} = 0.7 \text{ V}$$

$$I_E = (\beta + 1)I_B \cong I_C$$

$$I_C = \beta I_B$$

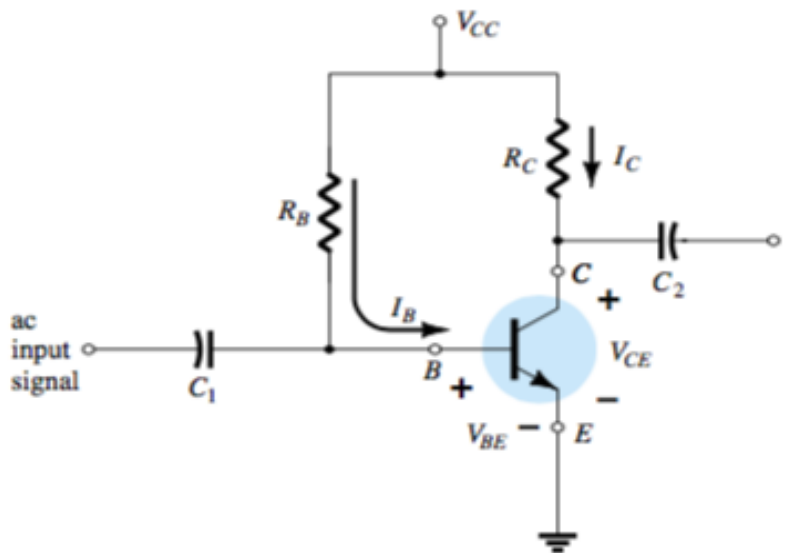

DC
Analysis

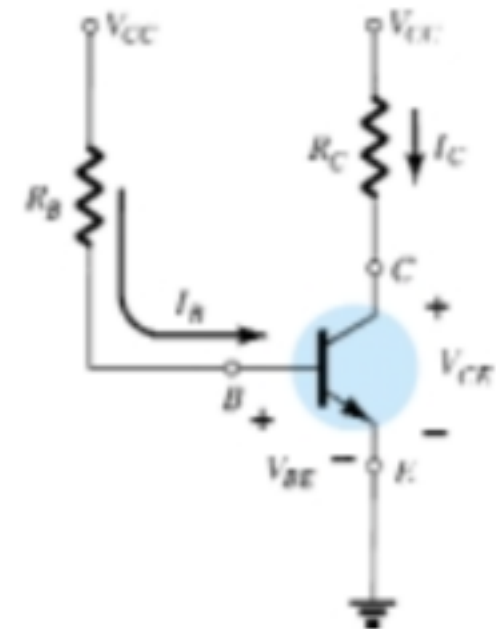




EEC2146: Electronic Circuits and Measurements

BJT Transistors

DC Analysis (Fixed Bias):

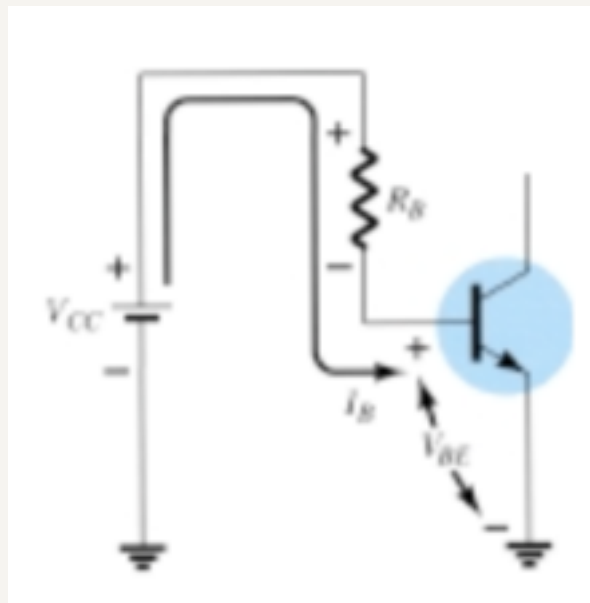

$$+V_{CC} - I_B R_B - V_{BE} = 0$$

$$I_B = \frac{V_{CC} - V_{BE}}{R_B}$$

$$I_C = \beta I_B$$

$$V_{BE} = 0.7 \text{ V}$$

$$I_E = (\beta + 1)I_B \cong I_C$$


$$I_C = \beta I_B$$



EEC2146: Electronic Circuits and Measurements

BJT Transistors

DC Analysis (Fixed Bias):

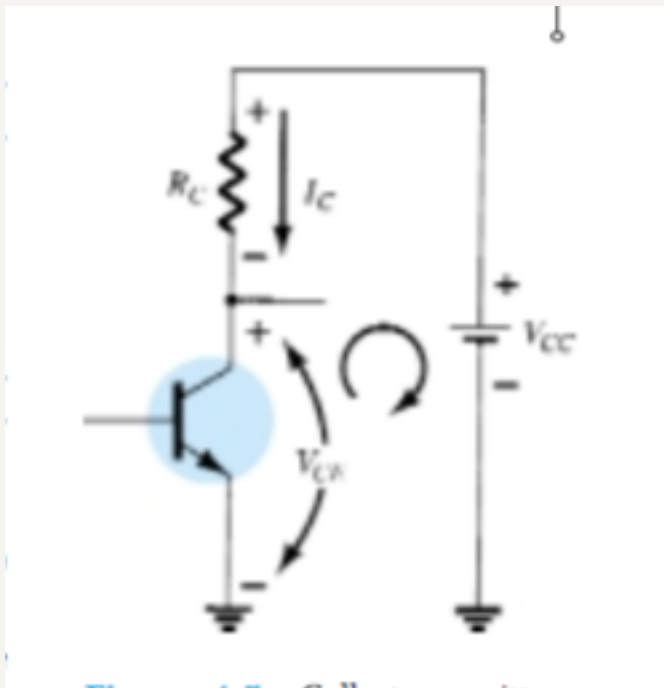

$$V_{BE} = 0.7 \text{ V}$$

$$I_E = (\beta + 1)I_B \cong I_C$$

$$I_C = \beta I_B$$

$$V_{CE} + I_C R_C - V_{CC} = 0$$

$$V_{CE} = V_{CC} - I_C R_C$$

$$V_{CE} = V_C - V_E$$

$$V_{CE} = V_C$$

$$V_{BE} = V_B - V_E$$



EEC2146: Electronic Circuits and Measurements

BJT Transistors

DC Analysis (Fixed Bias):

Determine the following for the fixed-bias configuration

- (a) I_{BQ} and I_{CQ} .
- (b) V_{CEQ} .
- (c) V_B and V_C .
- (d) V_{BC} .

$$V_{BE} = 0.7 \text{ V}$$

$$I_E = (\beta + 1)I_B \cong I_C$$

$$I_C = \beta I_B$$

$$I_{BQ} = \frac{V_{CC} - V_{BE}}{R_B} = \frac{12 \text{ V} - 0.7 \text{ V}}{240 \text{ k}\Omega} = 47.08 \text{ }\mu\text{A}$$


$$I_{CQ} = \beta I_{BQ} = (50)(47.08 \text{ }\mu\text{A}) = 2.35 \text{ mA}$$

$$\begin{aligned} V_{CEQ} &= V_{CC} - I_C R_C \\ &= 12 \text{ V} - (2.35 \text{ mA})(2.2 \text{ k}\Omega) \\ &= 6.83 \text{ V} \end{aligned}$$

$$V_B = V_{BE} = 0.7 \text{ V}$$

$$V_C = V_{CE} = 6.83 \text{ V}$$

$$\begin{aligned} V_{BC} &= V_B - V_C = 0.7 \text{ V} - 6.83 \text{ V} \\ &= -6.13 \text{ V} \end{aligned}$$

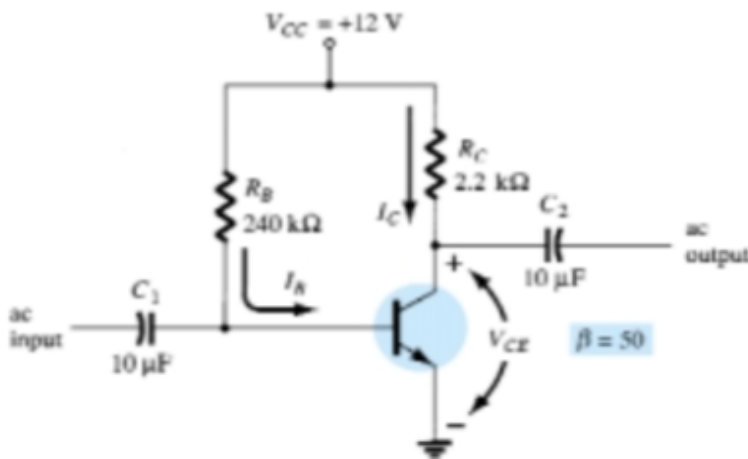



EEC2146: Electronic Circuits and Measurements


BJT Transistors

DC Analysis (Emitter Stabilized):

$$V_{BE} = 0.7 \text{ V}$$

$$I_E = (\beta + 1)I_B \cong I_C$$

$$I_C = \beta I_B$$

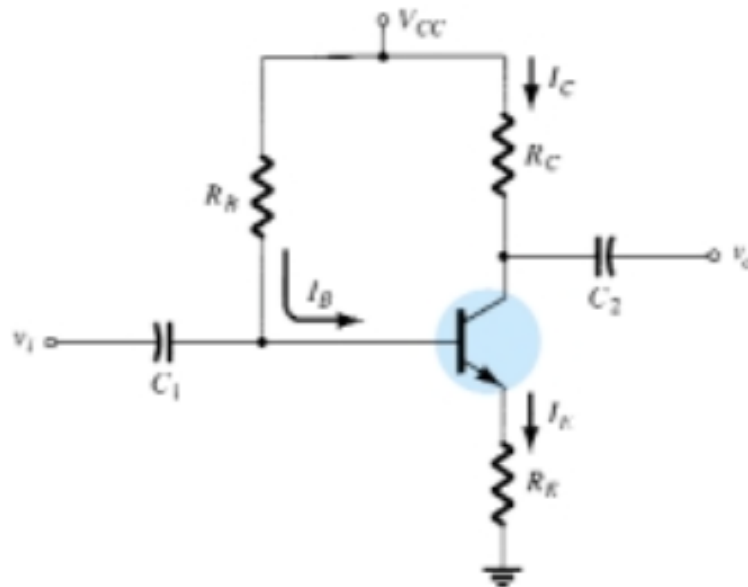




BJT Transistors

DC Analysis (Emitter Stabilized):

$$V_{BE} = 0.7 \text{ V}$$

$$I_E = (\beta + 1)I_B \cong I_C$$

$$I_C = \beta I_B$$

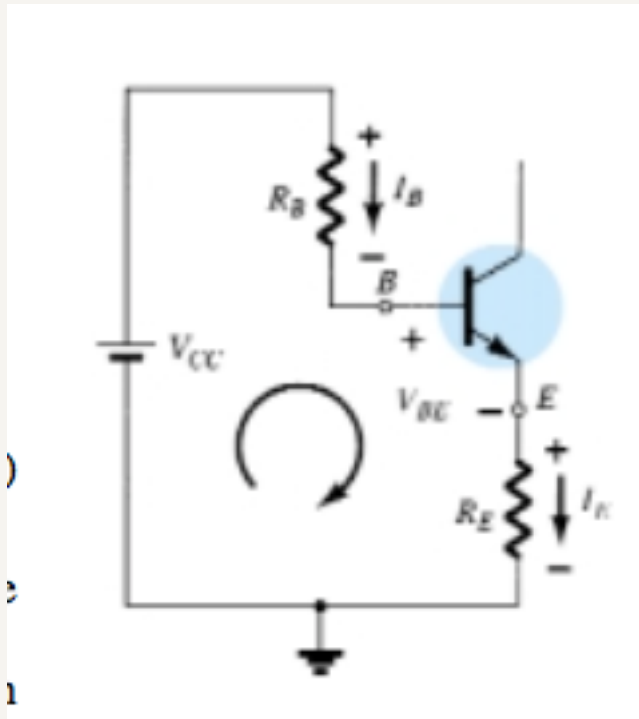

$$+V_{CC} - I_B R_B - V_{BE} - I_E R_E = 0$$

$$I_E = (\beta + 1)I_B$$

$$V_{CC} - I_B R_B - V_{BE} - (\beta + 1)I_B R_E = 0$$

$$-I_B(R_B + (\beta + 1)R_E) + V_{CC} - V_{BE} = 0$$

$$I_B(R_B + (\beta + 1)R_E) - V_{CC} + V_{BE} = 0$$
$$I_B(R_B + (\beta + 1)R_E) = V_{CC} - V_{BE}$$

$$I_B = \frac{V_{CC} - V_{BE}}{R_B + (\beta + 1)R_E}$$




BJT Transistors

DC Analysis (Emitter Stabilized):

$$V_{BE} = 0.7 \text{ V}$$

$$I_E = (\beta + 1)I_B \cong I_C$$

$$I_C = \beta I_B$$

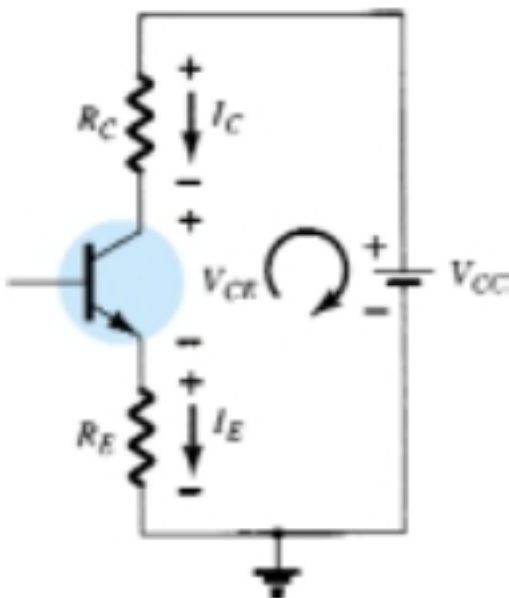

$$+I_E R_E + V_{CE} + I_C R_C - V_{CC} = 0$$

$$V_{CE} - V_{CC} + I_C(R_C + R_E) = 0$$

$$V_{CE} = V_{CC} - I_C(R_C + R_E)$$

$$V_E = I_E R_E$$

$$V_{CE} = V_C - V_E$$

$$V_C = V_{CE} + V_E$$

$$V_C = V_{CC} - I_C R_C$$

$$V_B = V_{CC} - I_B R_B$$

$$V_B = V_{BE} + V_E$$




EEC2146: Electronic Circuits and Measurements

BJT Transistors

DC Analysis (Emitter Stabilized):

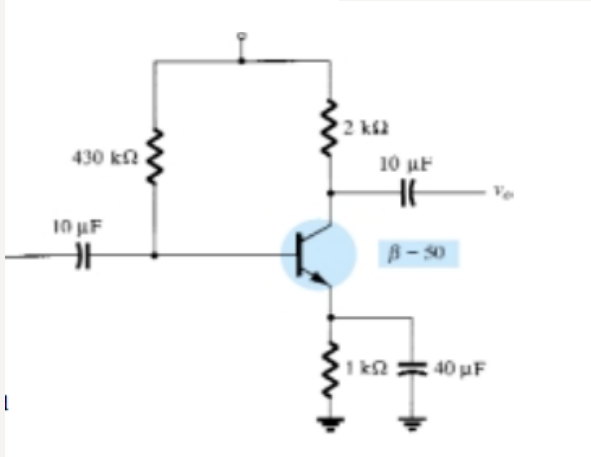- (a) I_B .
- (b) I_C .
- (c) V_{CE} .
- (d) V_C .
- (e) V_E .
- (f) V_B .
- (g) V_{BC} .



$$I_B = \frac{V_{CC} - V_{BE}}{R_B + (\beta + 1)R_E} = \frac{20 \text{ V} - 0.7 \text{ V}}{430 \text{ k}\Omega + (51)(1 \text{ k}\Omega)}$$

$$= \frac{19.3 \text{ V}}{481 \text{ k}\Omega} = 40.1 \mu\text{A}$$

$$I_C = \beta I_B$$

$$= (50)(40.1 \mu\text{A})$$

$$\cong 2.01 \text{ mA}$$

$$V_{CE} = V_{CC} - I_C(R_C + R_E)$$

$$= 20 \text{ V} - (2.01 \text{ mA})(2 \text{ k}\Omega + 1 \text{ k}\Omega) = 20 \text{ V} - 6.03 \text{ V}$$

$$= 13.97 \text{ V}$$



BJT Transistors


DC Analysis (Emitter Stabilized):

$$V_{BE} = 0.7 \text{ V}$$

$$I_E = (\beta + 1)I_B \cong I_C$$

$$I_C = \beta I_B$$

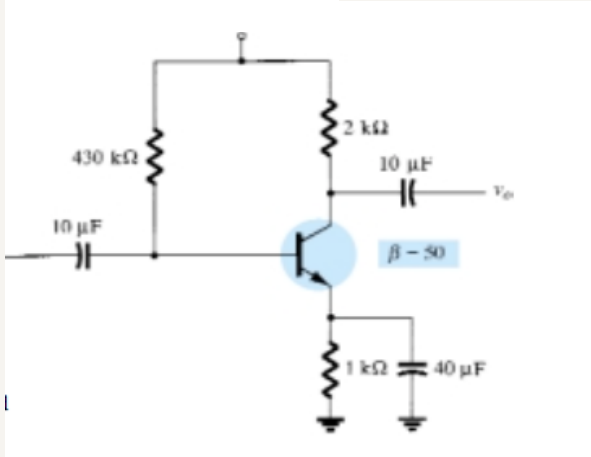- (a) I_B .
- (b) I_C .
- (c) V_{CE} .
- (d) V_C .
- (e) V_E .
- (f) V_B .
- (g) V_{BC} .



$$\begin{aligned} V_C &= V_{CC} - I_C R_C \\ &= 20 \text{ V} - (2.01 \text{ mA})(2 \text{ k}\Omega) = 20 \text{ V} - 4.02 \text{ V} \\ &= \mathbf{15.98 \text{ V}} \end{aligned}$$

$$\begin{aligned} V_E &= V_C - V_{CE} \\ &= 15.98 \text{ V} - 13.97 \text{ V} \\ &= \mathbf{2.01 \text{ V}} \end{aligned}$$

$$\begin{aligned} V_B &= V_{BE} + V_E \\ &= 0.7 \text{ V} + 2.01 \text{ V} \\ &= \mathbf{2.71 \text{ V}} \end{aligned}$$

$$\begin{aligned} V_{BC} &= V_B - V_C \\ &= 2.71 \text{ V} - 15.98 \text{ V} \\ &= \mathbf{-13.27 \text{ V}} \quad (\text{reverse-biased as required}) \end{aligned}$$



EEC2146: Electronic Circuits and Measurements


BJT Transistors

DC Analysis (Voltage Divider):

$$V_{BE} = 0.7 \text{ V}$$

$$I_E = (\beta + 1)I_B \cong I_C$$

$$I_C = \beta I_B$$

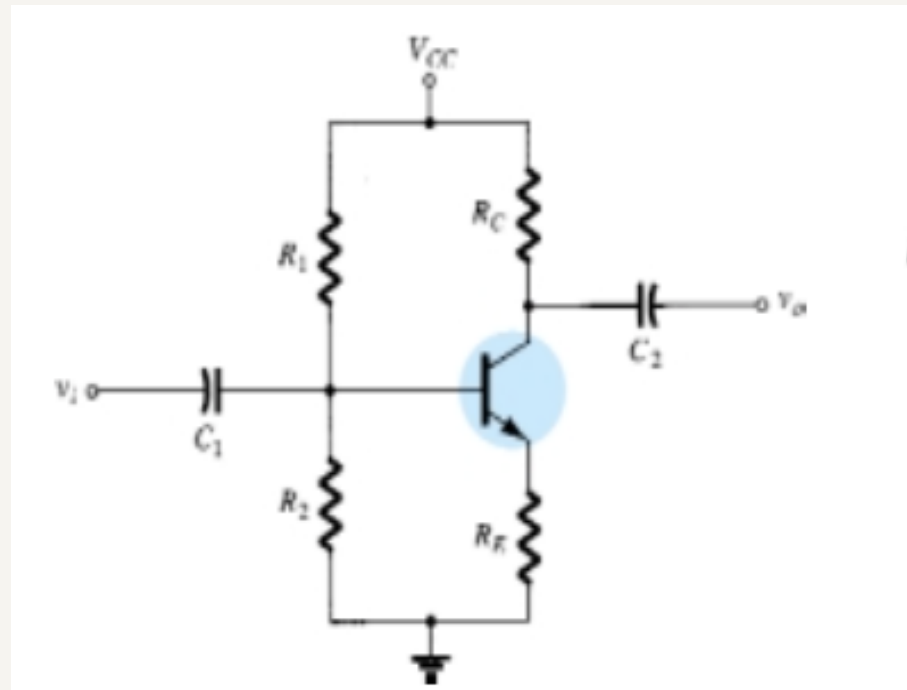



EEC2146: Electronic Circuits and Measurements



BJT Transistors

DC Analysis (Voltage Divider):


$$V_{BE} = 0.7 \text{ V}$$

$$I_E = (\beta + 1)I_B \cong I_C$$

$$I_C = \beta I_B$$

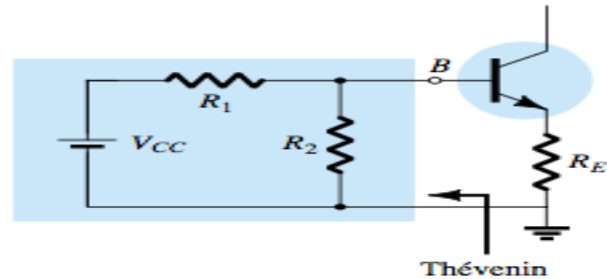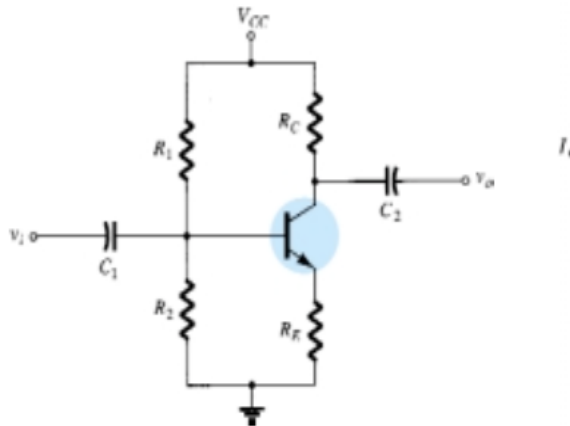

$$R_{Th} = R_1 || R_2$$

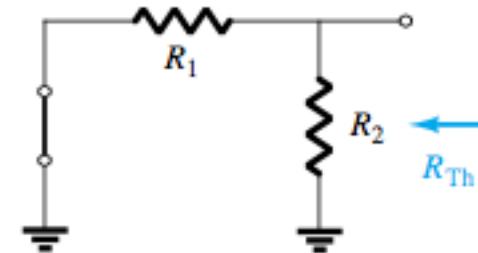



EEC2146: Electronic Circuits and Measurements


BJT Transistors

DC Analysis (Voltage Divider):


$$V_{BE} = 0.7 \text{ V}$$

$$I_E = (\beta + 1)I_B \cong I_C$$

$$I_C = \beta I_B$$

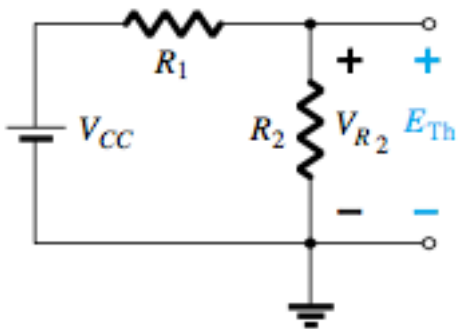
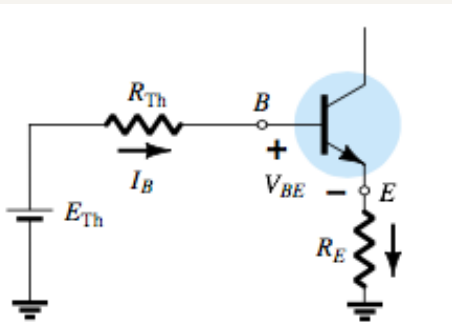
$$E_{Th} = V_{R_2} = \frac{R_2 V_{CC}}{R_1 + R_2}$$



$$I_B = \frac{E_{Th} - V_{BE}}{R_{Th} + (\beta + 1)R_E}$$

$$V_{CE} = V_{CC} - I_C(R_C + R_E)$$



EEC2146: Electronic Circuits and Measurements

BJT Transistors


DC Analysis (Voltage Divider):

Determine the dc bias voltage V_{CE} and the current I_C for the voltage-divider

$$V_{BE} = 0.7 \text{ V}$$

$$I_E = (\beta + 1)I_B \cong I_C$$

$$I_C = \beta I_B$$

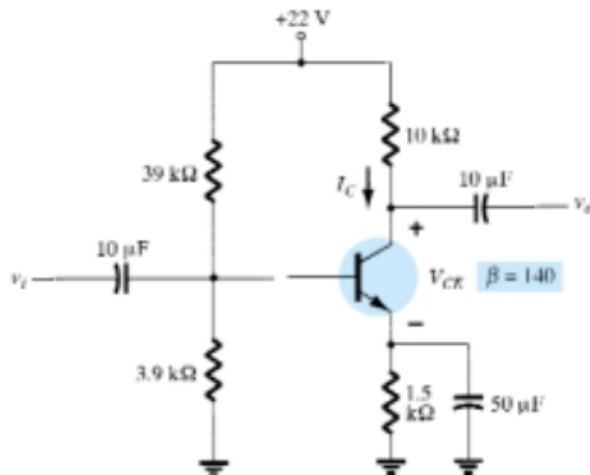

$$R_{Th} = R_1 \parallel R_2$$

$$= \frac{(39 \text{ k}\Omega)(3.9 \text{ k}\Omega)}{39 \text{ k}\Omega + 3.9 \text{ k}\Omega} = 3.55 \text{ k}\Omega$$

$$E_{Th} = \frac{R_2 V_{CC}}{R_1 + R_2}$$

$$= \frac{(3.9 \text{ k}\Omega)(22 \text{ V})}{39 \text{ k}\Omega + 3.9 \text{ k}\Omega} = 2 \text{ V}$$




EEC2146: Electronic Circuits and Measurements

BJT Transistors

DC Analysis (Voltage Divider):

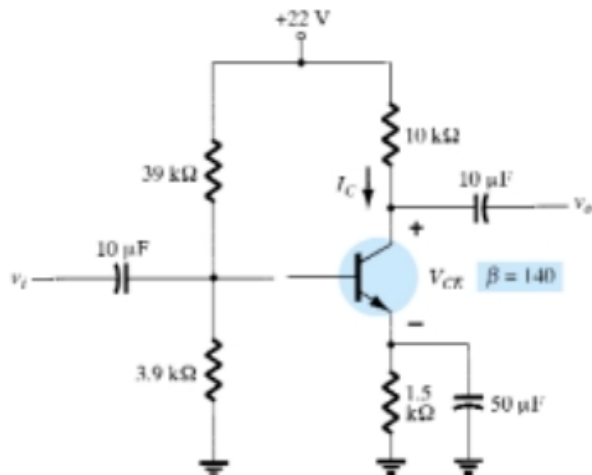Determine the dc bias voltage V_{CE} and the current I_C for the voltage-divider



$$\begin{aligned}
 I_B &= \frac{E_{Th} - V_{BE}}{R_{Th} + (\beta + 1)R_E} \\
 &= \frac{2 \text{ V} - 0.7 \text{ V}}{3.55 \text{ k}\Omega + (141)(1.5 \text{ k}\Omega)} = \frac{1.3 \text{ V}}{3.55 \text{ k}\Omega + 211.5 \text{ k}\Omega} \\
 &= 6.05 \mu\text{A} \\
 I_C &= \beta I_B \\
 &= (140)(6.05 \mu\text{A}) \\
 &= 0.85 \text{ mA}
 \end{aligned}$$

$$\begin{aligned}
 V_{CE} &= V_{CC} - I_C(R_C + R_E) \\
 &= 22 \text{ V} - (0.85 \text{ mA})(10 \text{ k}\Omega + 1.5 \text{ k}\Omega) \\
 &= 22 \text{ V} - 9.78 \text{ V} \\
 &= 12.22 \text{ V}
 \end{aligned}$$



EEC2146: Electronic Circuits and Measurements



BJT Transistors

DC Analysis (Voltage Feedback):

$$V_{BE} = 0.7 \text{ V}$$

$$I_E = (\beta + 1)I_B \cong I_C$$

$$I_C = \beta I_B$$

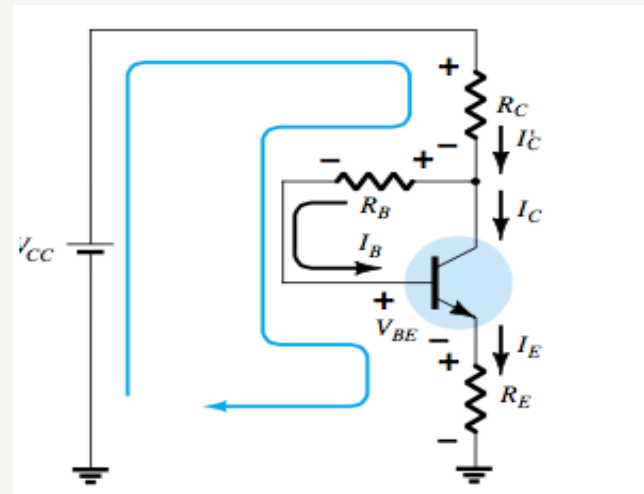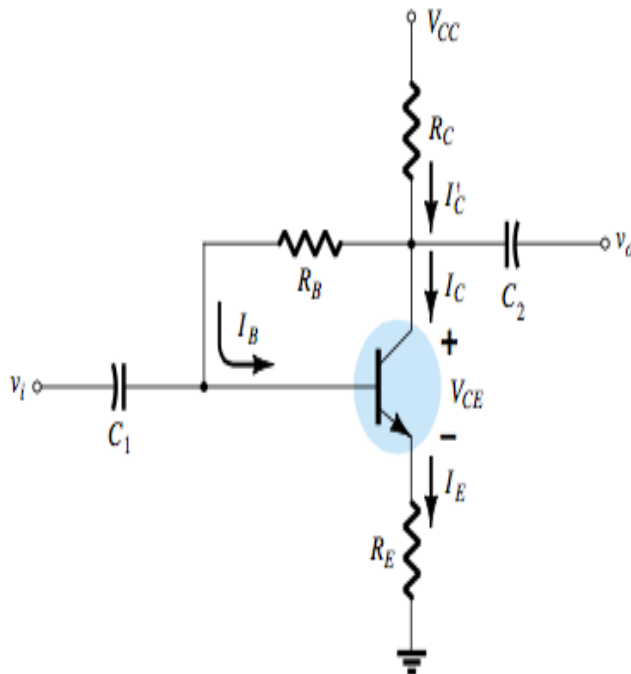

$$V_{CC} - I_C' R_C - I_B R_B - V_{BE} - I_E R_E = 0$$

$$V_{CC} - \beta I_B R_C - I_B R_B - V_{BE} - \beta I_B R_E = 0$$



EEC2146: Electronic Circuits and Measurements



BJT Transistors

DC Analysis (Voltage Feedback):

$$V_{BE} = 0.7 \text{ V}$$

$$I_E = (\beta + 1)I_B \cong I_C$$

$$I_C = \beta I_B$$

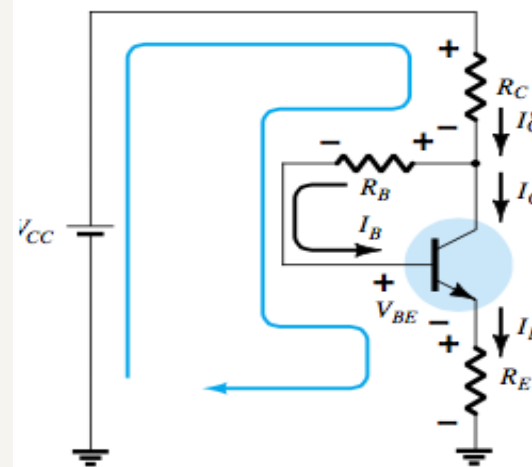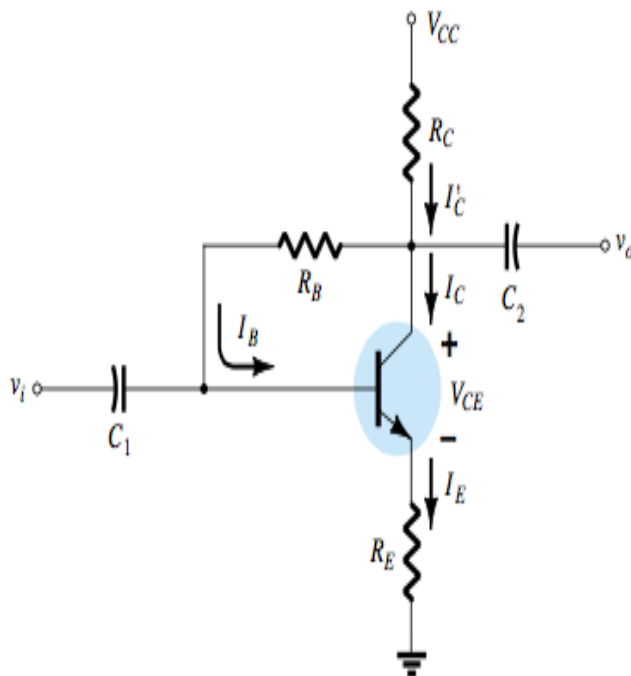

$$I_B = \frac{V_{CC} - V_{BE}}{R_B + \beta(R_C + R_E)}$$



EEC2146: Electronic Circuits and Measurements



BJT Transistors

DC Analysis (Voltage Feedback):

$$V_{BE} = 0.7 \text{ V}$$

$$I_E = (\beta + 1)I_B \cong I_C$$

$$I_C = \beta I_B$$

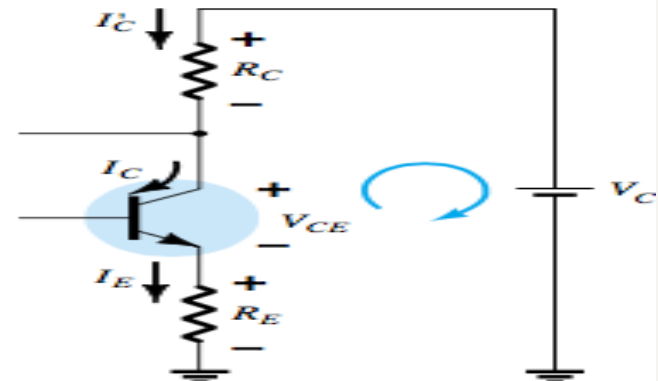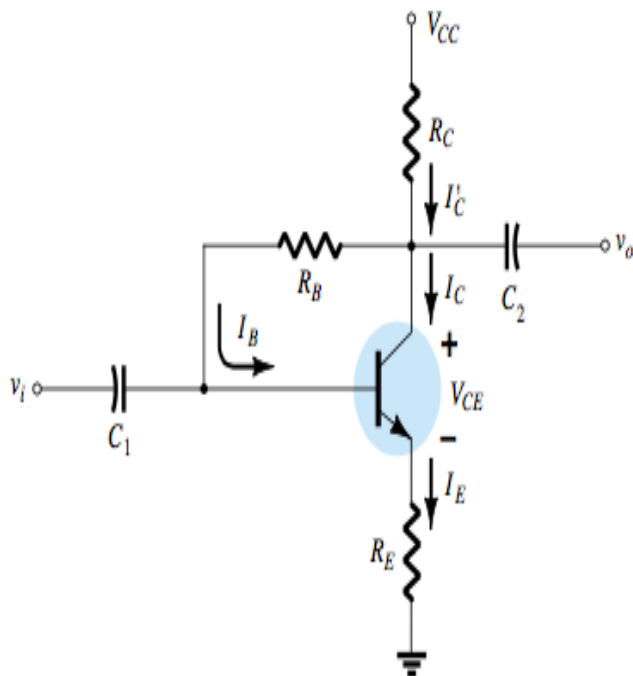

$$I_E R_E + V_{CE} + I_C' R_C - V_{CC} = 0$$

$$I_C (R_C + R_E) + V_{CE} - V_{CC} = 0$$

$$V_{CE} = V_{CC} - I_C (R_C + R_E)$$



EEC2146: Electronic Circuits and Measurements


BJT Transistors

DC Analysis (Voltage Feedback):

$$V_{BE} = 0.7 \text{ V}$$

$$I_E = (\beta + 1)I_B \cong I_C$$

$$I_C = \beta I_B$$

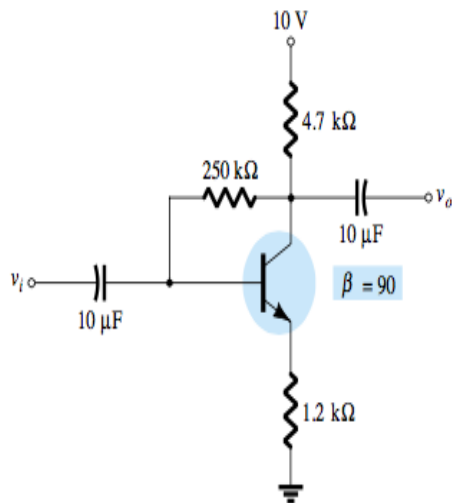

$$\begin{aligned} I_B &= \frac{V_{CC} - V_{BE}}{R_B + \beta(R_C + R_E)} \\ &= \frac{10 \text{ V} - 0.7 \text{ V}}{250 \text{ k}\Omega + (90)(4.7 \text{ k}\Omega + 1.2 \text{ k}\Omega)} \\ &= \frac{9.3 \text{ V}}{250 \text{ k}\Omega + 531 \text{ k}\Omega} = \frac{9.3 \text{ V}}{781 \text{ k}\Omega} \\ &= 11.91 \mu\text{A} \end{aligned}$$

$$\begin{aligned} V_{CEQ} &= V_{CC} - I_C(R_C + R_E) \\ &= 10 \text{ V} - (1.07 \text{ mA})(4.7 \text{ k}\Omega + 1.2 \text{ k}\Omega) \\ &= 10 \text{ V} - 6.31 \text{ V} \\ &= 3.69 \text{ V} \end{aligned}$$

$$\begin{aligned} I_{CQ} &= \beta I_B = (90)(11.91 \mu\text{A}) \\ &= 1.07 \text{ mA} \end{aligned}$$



Break



BJT Transistors

AC Analysis : **THE r_e TRANSISTOR MODEL**

Common Base Amplifier

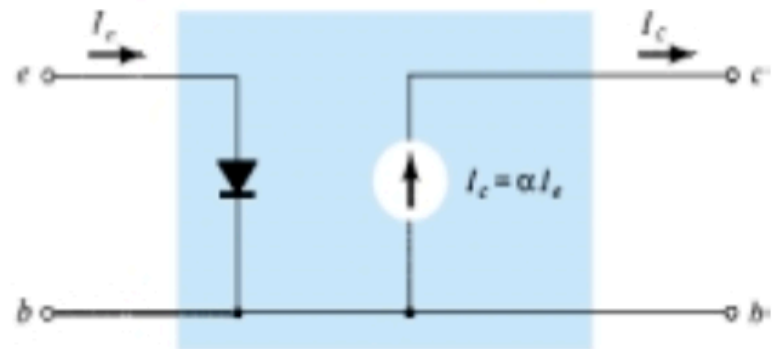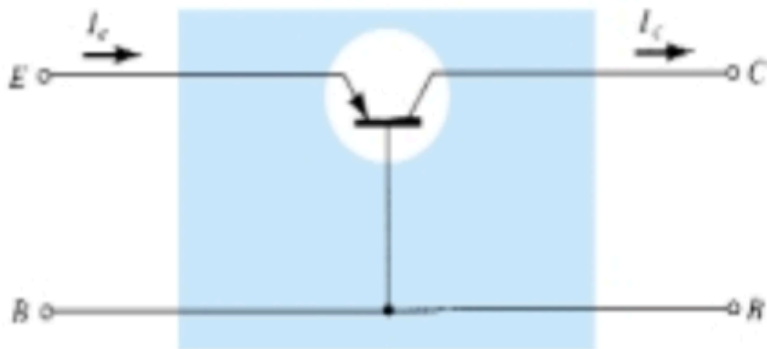





BJT Transistors

AC Analysis : **THE r_e TRANSISTOR MODEL**

Common Base Amplifier

$$r_e = \frac{26 \text{ mV}}{I_E}$$

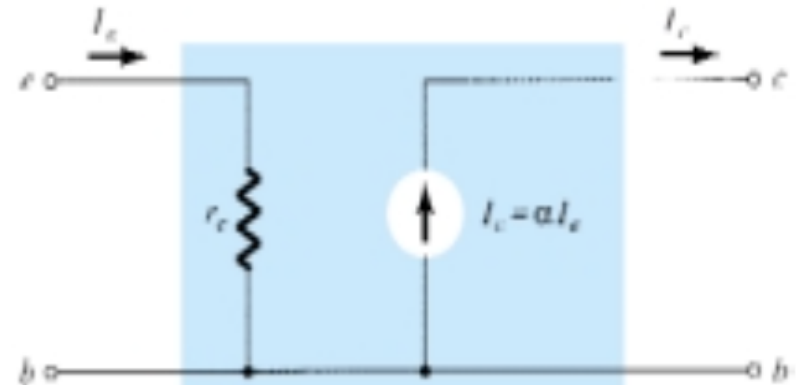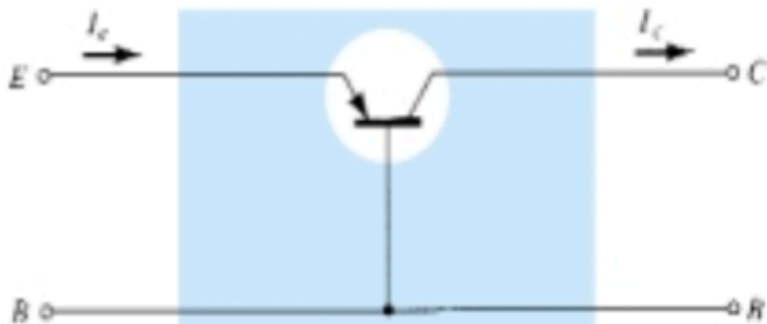





BJT Transistors

AC Analysis : **THE r_e TRANSISTOR MODEL**

Common Emitter Amplifier

$$r_e = \frac{26 \text{ mV}}{I_E}$$

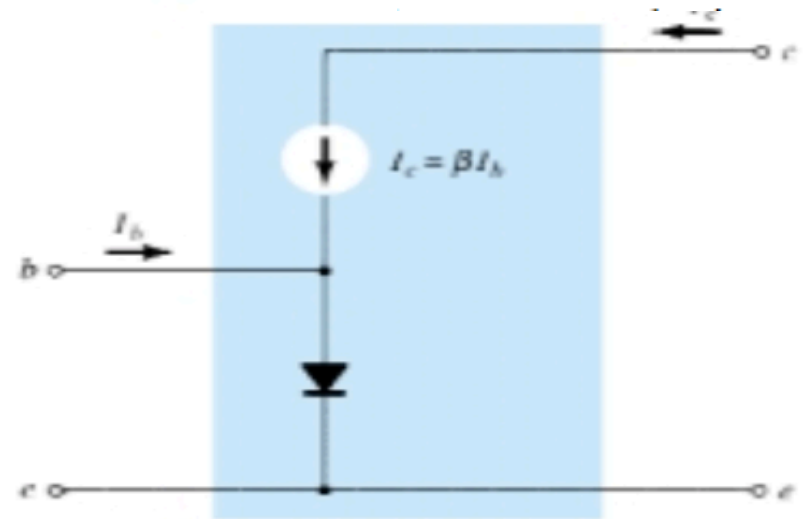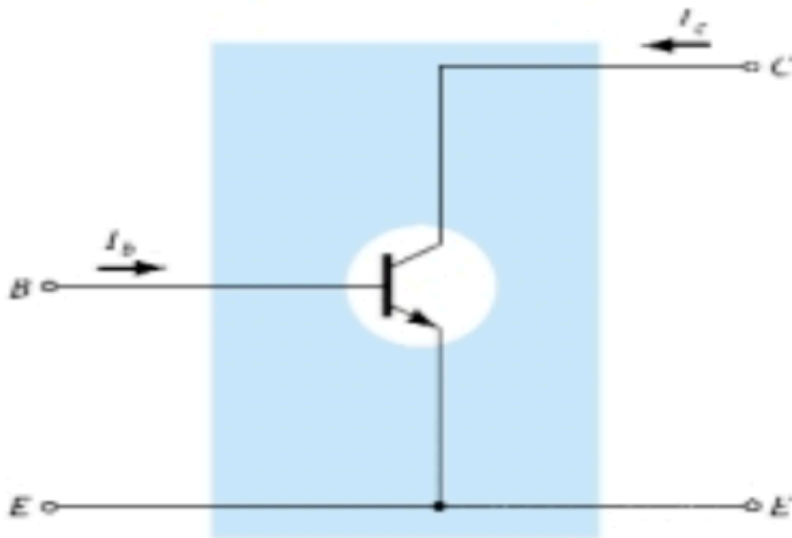





EEC2146: Electronic Circuits and Measurements

BJT Transistors

AC Analysis : **THE r_e TRANSISTOR MODEL**

Common Emitter Amplifier

$$r_e = \frac{26 \text{ mV}}{I_E}$$

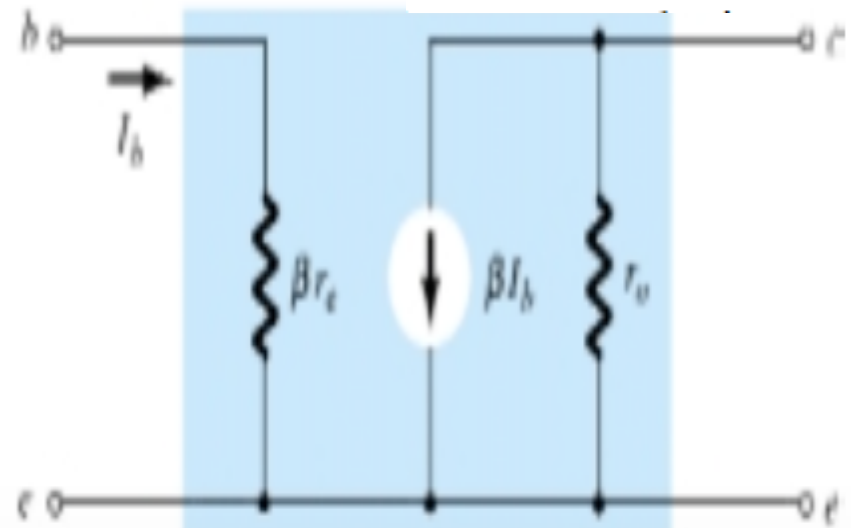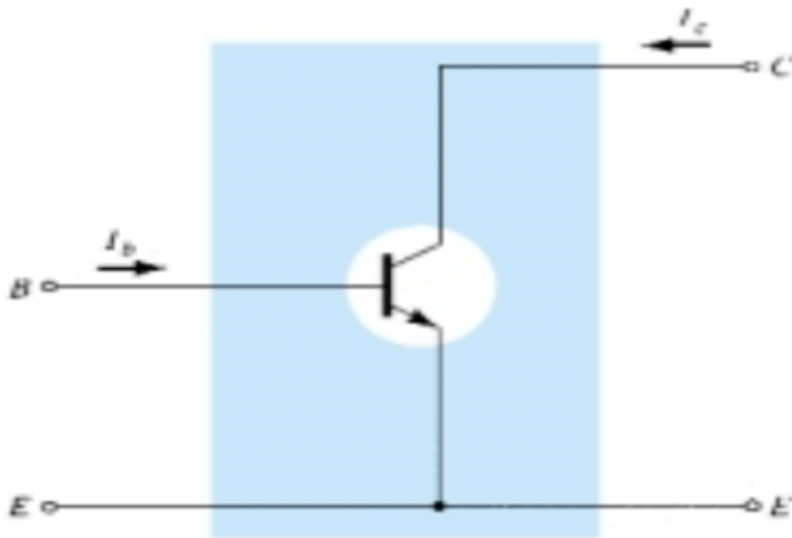



BJT Transistors

Steps of AC Analysis :

1- Perform DC Analysis to find I_E and r_e .

$$r_e = \frac{26 \text{ mV}}{I_E}$$

2- Put all capacitors short circuit.

3- Put all DC sources short circuit.

4- Draw the AC model.


5- Find Z_i , Z_o , A_v , A_i .



EEC2146: Electronic Circuits and Measurements

BJT Transistors


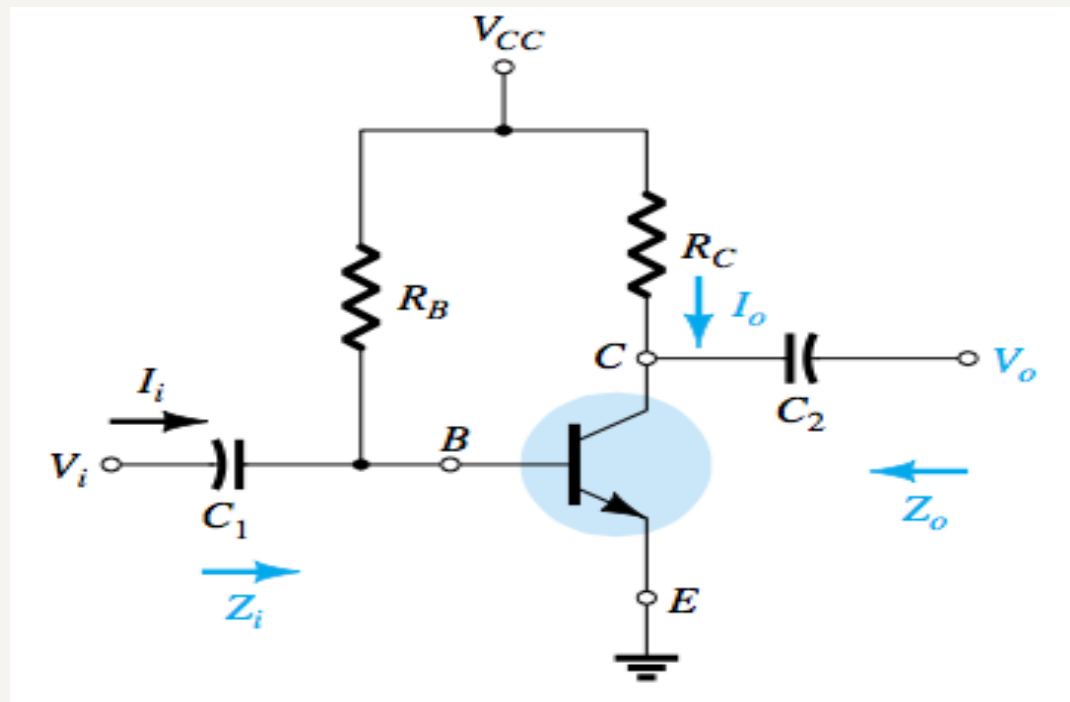
AC Analysis: COMMON-EMITTER FIXED-BIAS CONFIGURATION.





BJT Transistors

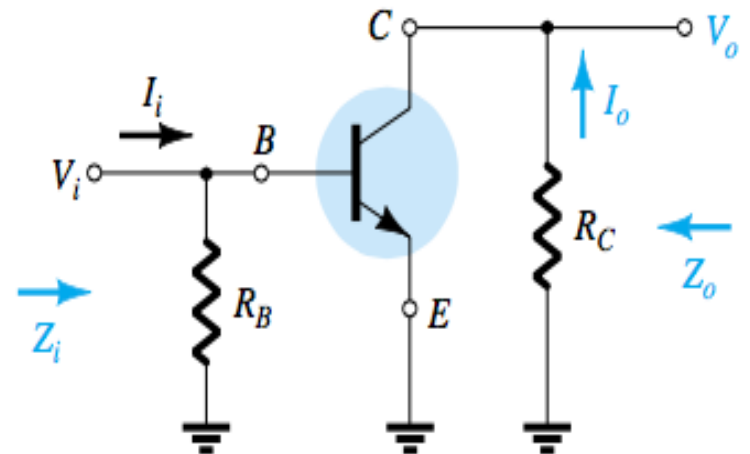
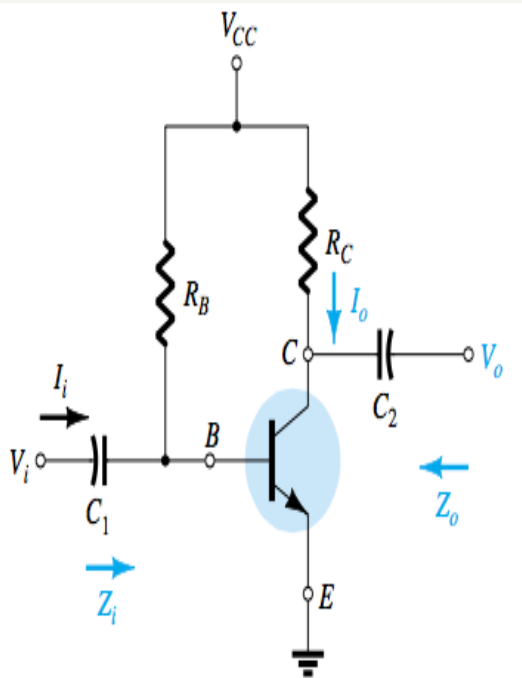
AC Analysis: COMMON-EMITTER FIXED-BIAS CONFIGURATION.





BJT Transistors

AC Analysis: COMMON-EMITTER FIXED-BIAS CONFIGURATION.

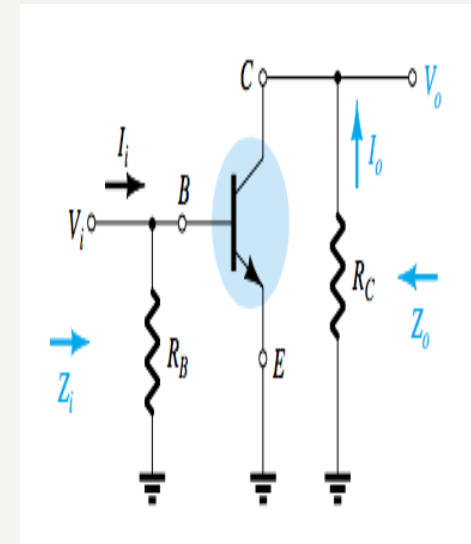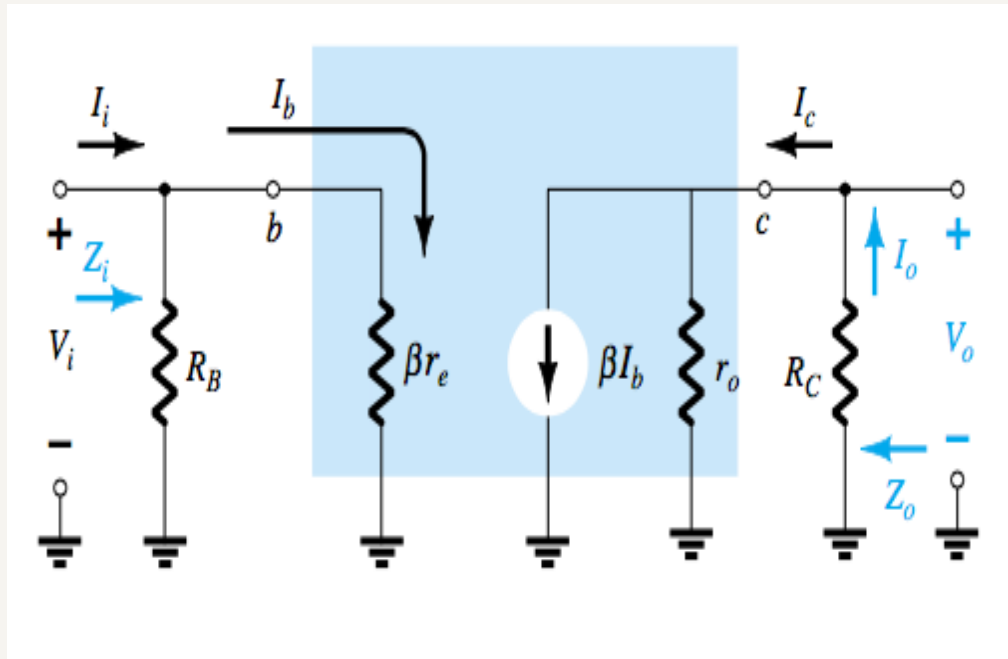




EEC2146: Electronic Circuits and Measurements

BJT Transistors

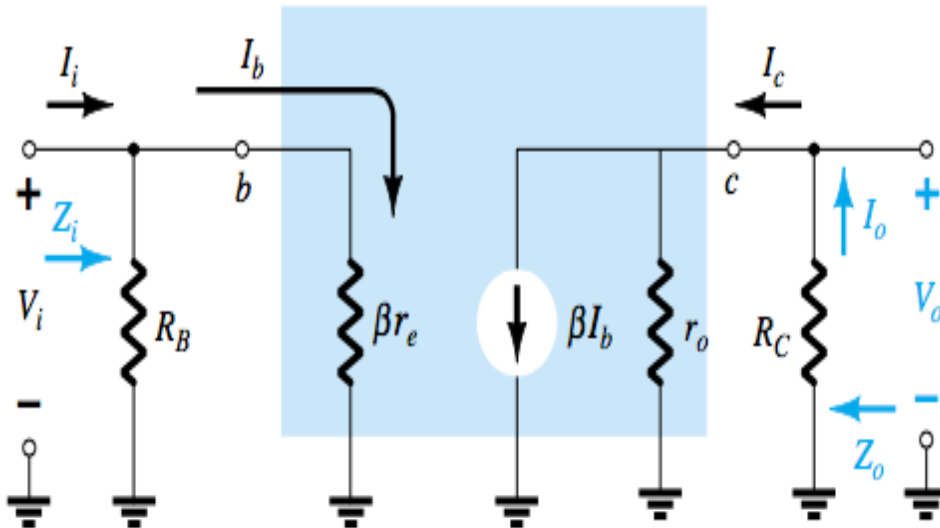AC Analysis: **COMMON-EMITTER FIXED-BIAS CONFIGURATION.**




$$Z_i = R_B \parallel \beta r_e$$



EEC2146: Electronic Circuits and Measurements


BJT Transistors

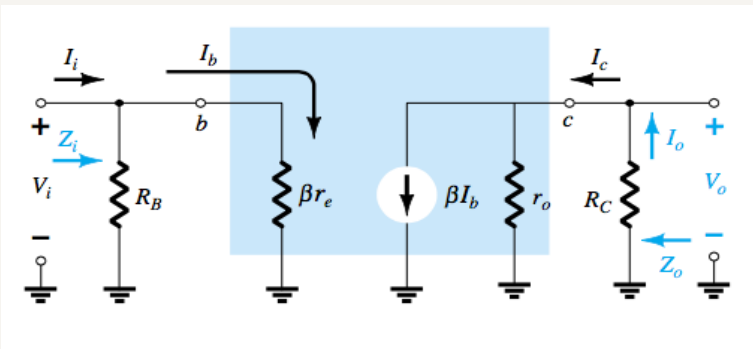AC Analysis: COMMON-EMITTER FIXED-BIAS CONFIGURATION.



To find Z_o

$$\vec{V}_i = 0, I_i = I_b = 0,$$

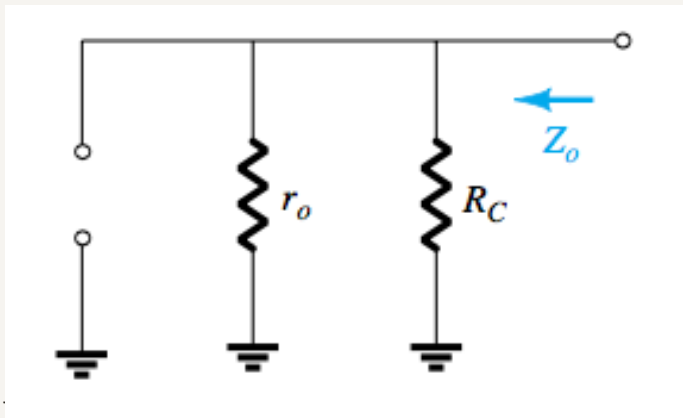


$$Z_o = R_C \parallel r_o$$



EEC2146: Electronic Circuits and Measurements

BJT Transistors

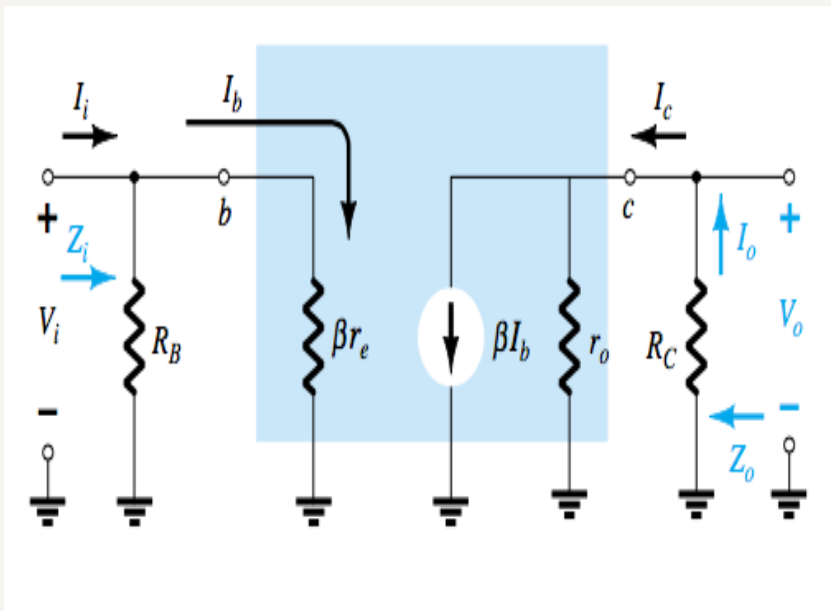AC Analysis: **COMMON-EMITTER FIXED-BIAS CONFIGURATION.**



$$V_o = -\beta I_b (R_C \parallel r_o)$$

$$I_b = \frac{V_i}{\beta r_c}$$

$$V_o = -\beta \left(\frac{V_i}{\beta r_e} \right) (R_C \parallel r_o)$$

$$A_v = \frac{V_o}{V_i} = -\frac{(R_C \parallel r_o)}{r_e}$$

$$A_i = -A_v \frac{Z_i}{R_C}$$




EEC2146: Electronic Circuits and Measurements

BJT Transistors


AC Analysis: COMMON-EMITTER FIXED-BIAS CONFIGURATION.

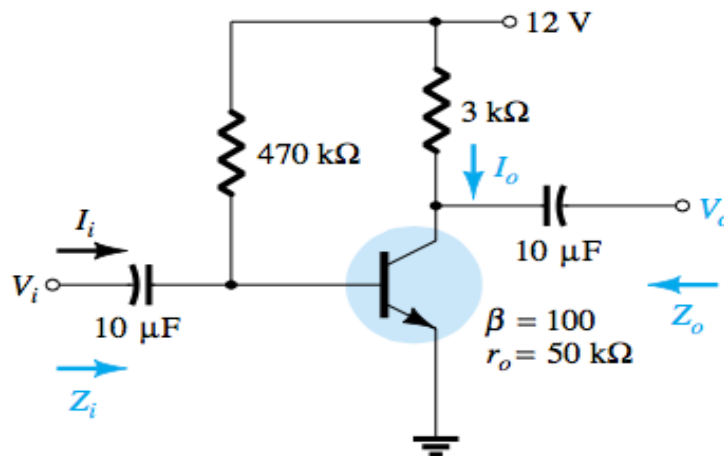- (a) Determine r_e .
- (b) Find Z_i (with $r_o = \infty \Omega$).
- (c) Calculate Z_o (with $r_o = \infty \Omega$).
- (d) Determine A_v (with $r_o = \infty \Omega$).
- (e) Find A_i (with $r_o = \infty \Omega$).
- (f) Repeat parts (c) through (e) including $r_o = 50 \text{ k}\Omega$ in all calculations and compare results.



BJT Transistors

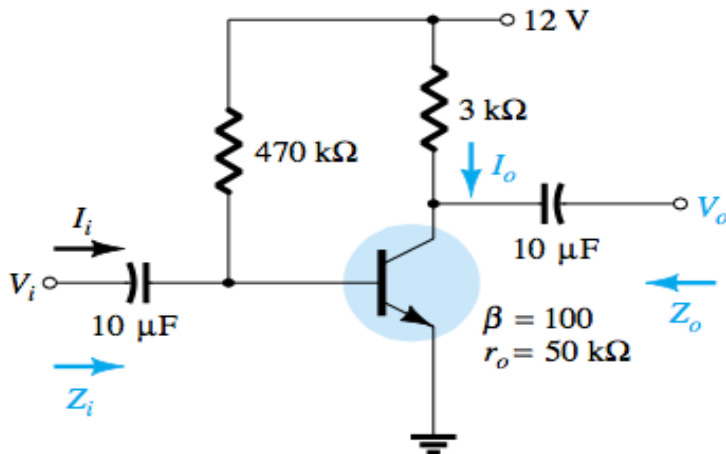AC Analysis: COMMON-EMITTER FIXED-BIAS CONFIGURATION.



DC analysis:

$$I_B = \frac{V_{CC} - V_{BE}}{R_B} = \frac{12 \text{ V} - 0.7 \text{ V}}{470 \text{ k}\Omega} = 24.04 \mu\text{A}$$

$$I_E = (\beta + 1)I_B = (101)(24.04 \mu\text{A}) = 2.428 \text{ mA}$$

$$r_e = \frac{26 \text{ mV}}{I_E} = \frac{26 \text{ mV}}{2.428 \text{ mA}} = 10.71 \Omega$$

$$\beta r_e = (100)(10.71 \Omega) = 1.071 \text{ k}\Omega$$

$$Z_i = R_B \parallel \beta r_e = 470 \text{ k}\Omega \parallel 1.071 \text{ k}\Omega = 1.069 \text{ k}\Omega$$

$$Z_o = R_C = 3 \text{ k}\Omega$$

$$A_v = -\frac{R_C}{r_e} = -\frac{3 \text{ k}\Omega}{10.71 \Omega} = -280.11$$


$$\text{Since } R_B \geq 10\beta r_e (470 \text{ k}\Omega > 10.71 \text{ k}\Omega)$$

$$A_i \cong \beta = 100$$



BJT Transistors

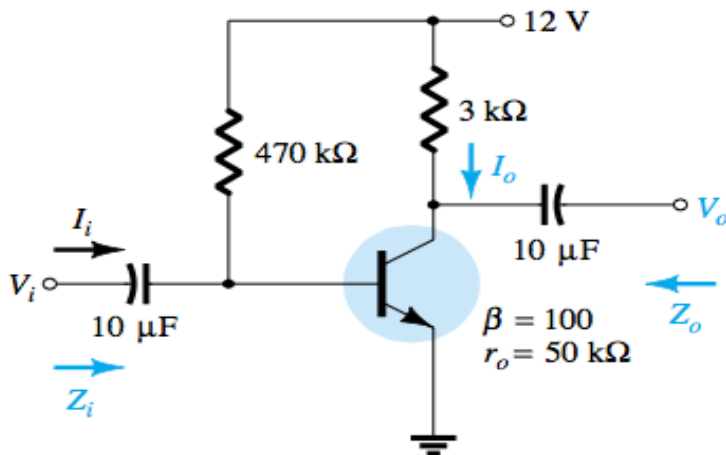AC Analysis: COMMON-EMITTER FIXED-BIAS CONFIGURATION.



$$Z_o = r_o \parallel R_C = 50 \text{ k}\Omega \parallel 3 \text{ k}\Omega = \mathbf{2.83 \text{ k}\Omega} \text{ vs. } 3 \text{ k}\Omega$$

$$A_v = -\frac{r_o \parallel R_C}{r_e} = \frac{2.83 \text{ k}\Omega}{10.71 \Omega} = \mathbf{-264.24} \text{ vs. } -280.11$$

$$A_i = \frac{\beta R_B r_o}{(r_o + R_C)(R_B + \beta r_e)} = \frac{(100)(470 \text{ k}\Omega)(50 \text{ k}\Omega)}{(50 \text{ k}\Omega + 3 \text{ k}\Omega)(470 \text{ k}\Omega + 1.071 \text{ k}\Omega)} = \mathbf{94.13} \text{ vs. } 100$$

As a check:


$$A_i = -A_v \frac{Z_i}{R_C} = \frac{-(-264.24)(1.069 \text{ k}\Omega)}{3 \text{ k}\Omega} = \mathbf{94.16}$$



EEC2146: Electronic Circuits and Measurements

BJT Transistors


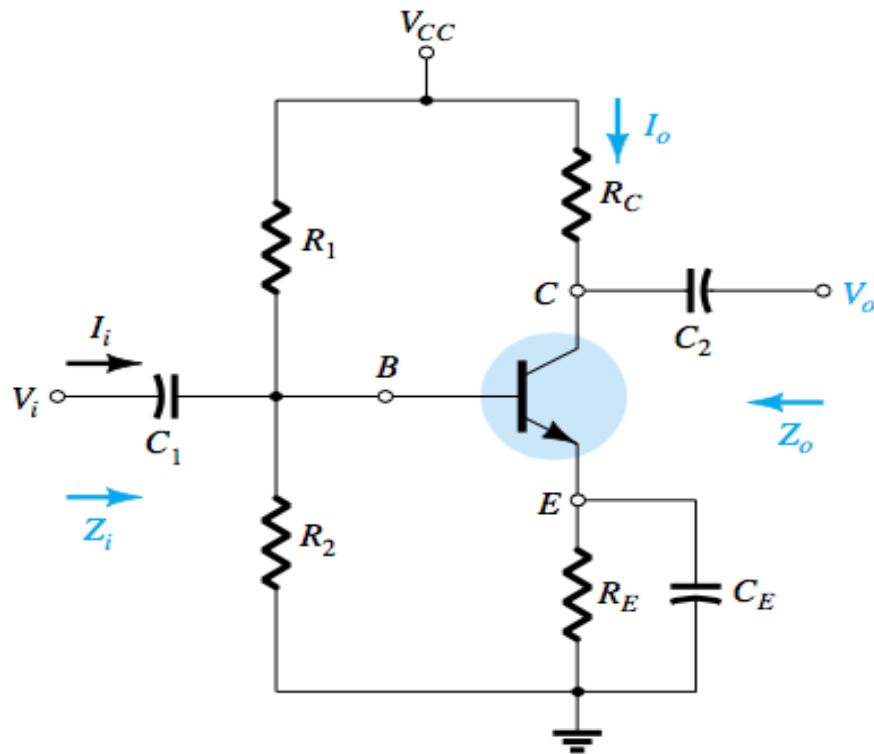
AC Analysis: **COMMON-EMITTER Voltage Divider** **CONFIGURATION.**





BJT Transistors

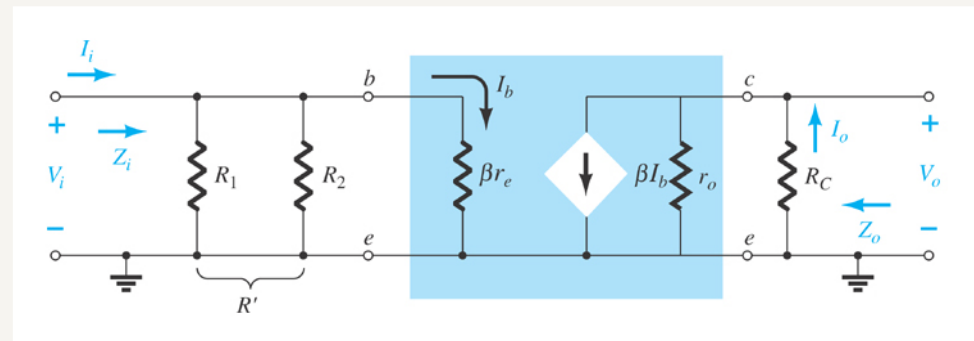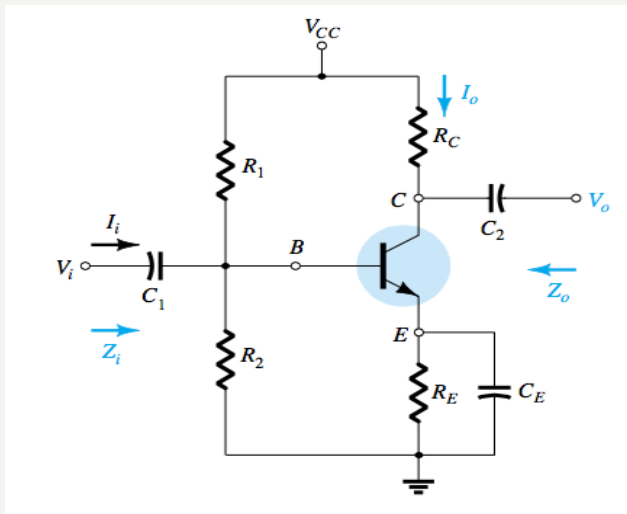
AC Analysis: COMMON-EMITTER Voltage Divider CONFIGURATION.





BJT Transistors

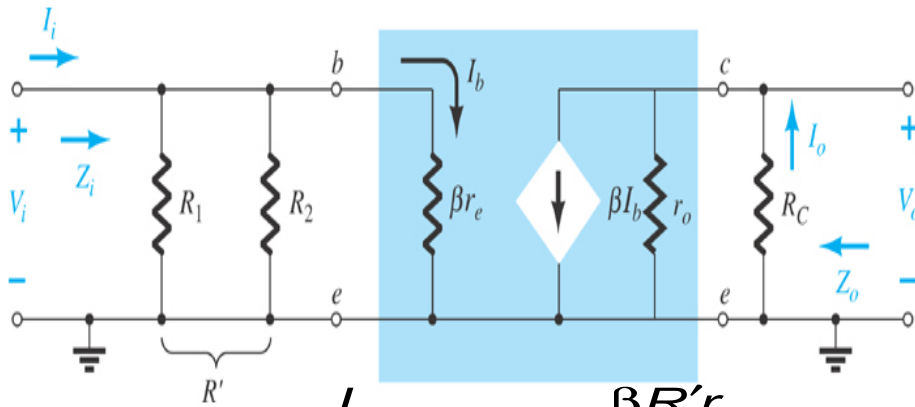AC Analysis: COMMON-EMITTER Voltage Divider CONFIGURATION.



$$A_i = \frac{I_o}{I_i} = \frac{\beta R' r_o}{(r_o + R_C)(R' + \beta r_e)}$$

$$A_i = \frac{I_o}{I_i} \cong \frac{\beta R'}{R' + \beta r_e} \Big|_{r_o \geq 10 R_C}$$

$$A_i = \frac{I_o}{I_i} \cong \beta \Big|_{r_o \geq 10 R_C, R' \geq 10 \beta r_e}$$

$$R' = R_1 \parallel R_2$$

$$Z_i = R' \parallel \beta r_e$$

$$Z_o = R_C \parallel r_o$$

$$Z_o \cong R_C \Big|_{r_o \geq 10 R_C}$$

$$A_v = \frac{V_o}{V_i} = \frac{-R_C \parallel r_o}{r_e}$$



$$A_v = \frac{V_o}{V_i} \cong -\frac{R_C}{r_e} \Big|_{r_o \geq 10 R_C}$$



EEC2146: Electronic Circuits and Measurements

BJT Transistors

AC Analysis: **CE EMITTER-BIAS CONFIGURATION**

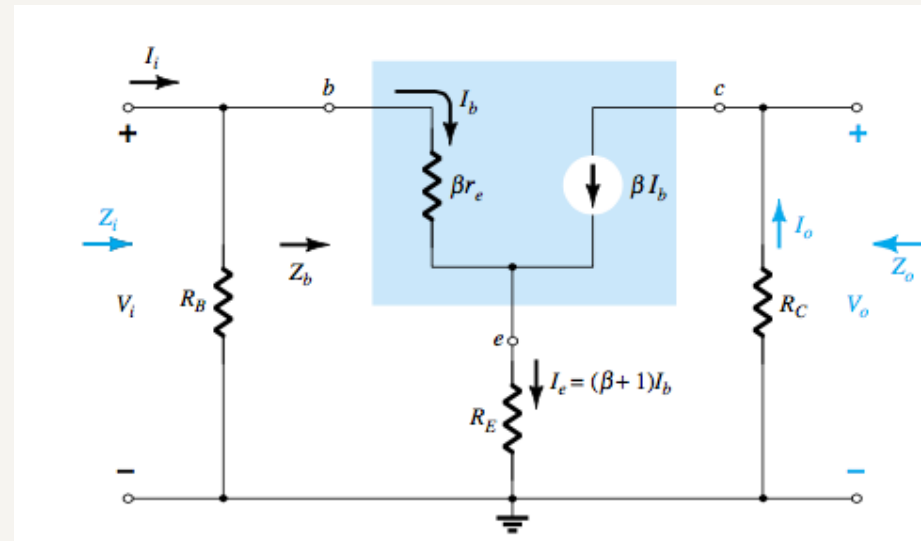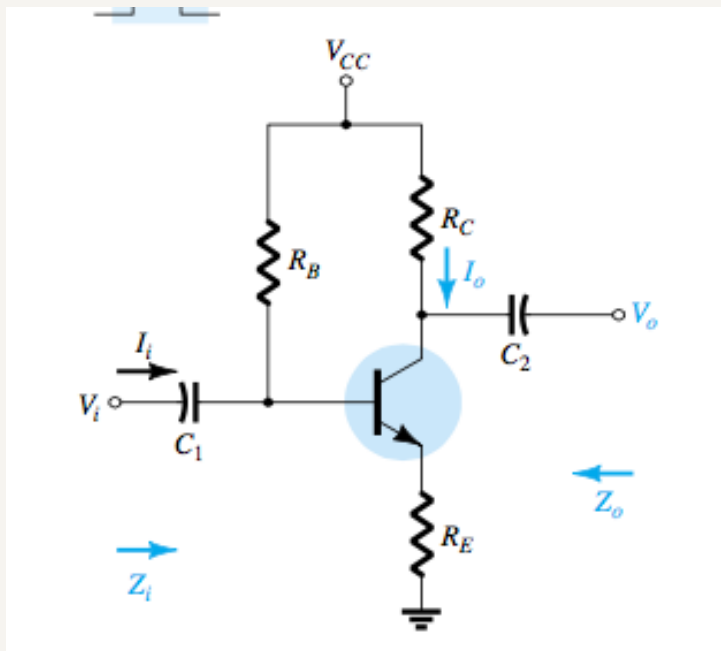




EEC2146: Electronic Circuits and Measurements

BJT Transistors

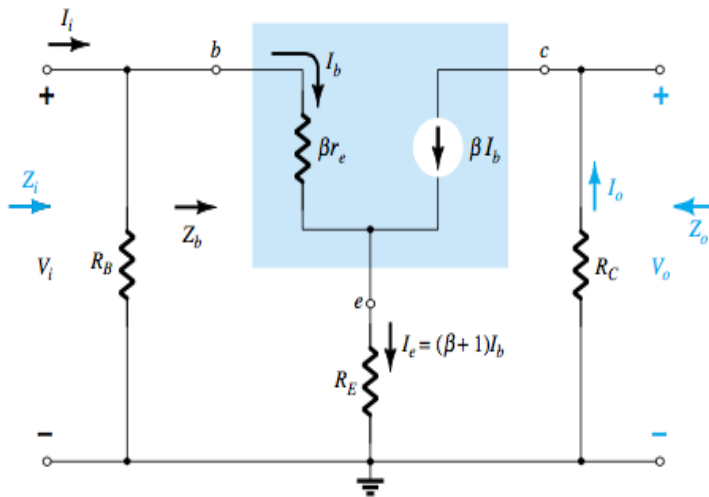AC Analysis: **CE EMITTER-BIAS CONFIGURATION**



$$Z_b = \beta r_e + (\beta + 1)R_E$$

$$Z_b \cong \beta(r_e + R_E)$$

$$Z_i = R_B \parallel Z_b$$

$$Z_o = R_C$$

$$A_v = \frac{V_o}{V_i} = -\frac{\beta R_C}{Z_b}$$



$$A_i = -A_v \frac{Z_i}{R_C}$$



EEC2146: Electronic Circuits and Measurements

BJT Transistors

AC Analysis: **Emitter follower (common collector)**

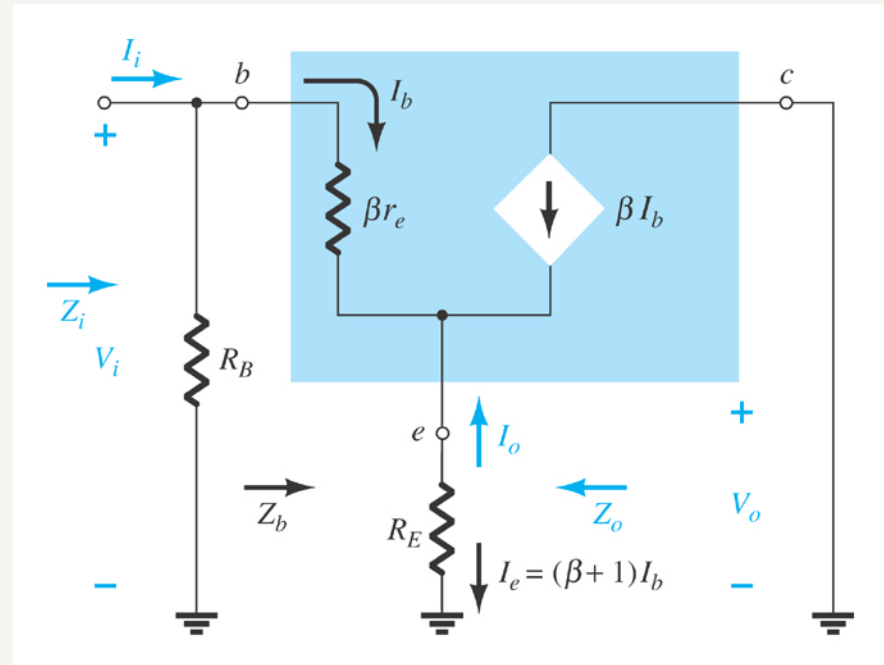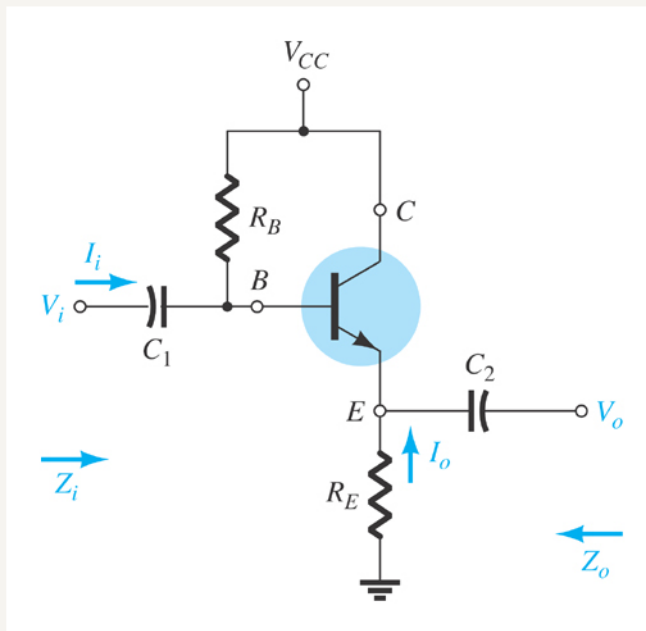




EEC2146: Electronic Circuits and Measurements

BJT Transistors

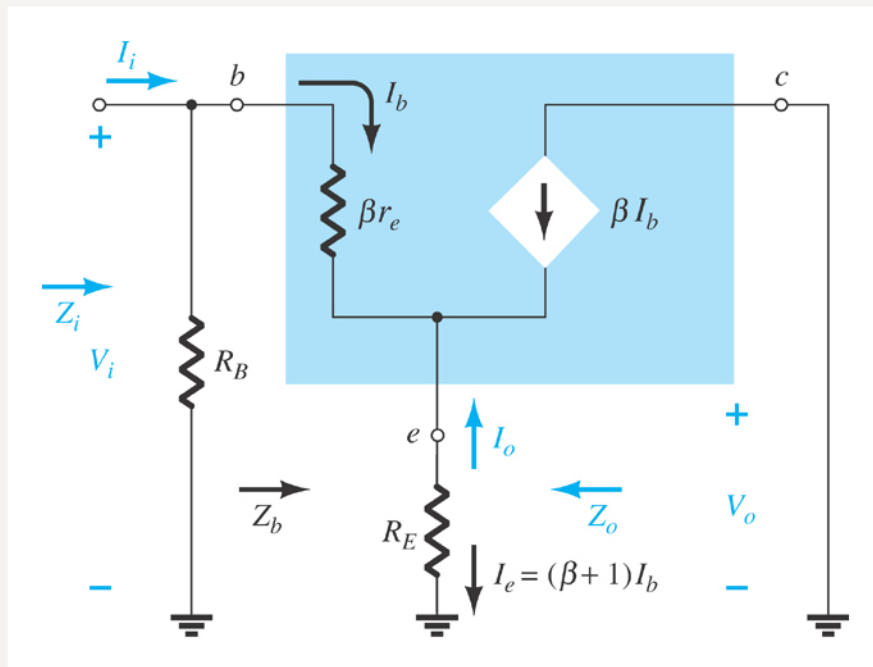AC Analysis: **Emitter follower (common collector)**



$$Z_i = R_B \parallel Z_b$$

$$Z_b \cong \beta R_E$$

$$Z_o = R_E \parallel r_e$$

$$A_v = \frac{V_o}{V_i} = \frac{R_E}{R_E + r_e}$$



$$A_i = -A_v \frac{Z_i}{R_E}$$



EEC2146: Electronic Circuits and Measurements

BJT Transistors

AC Analysis: Common Base

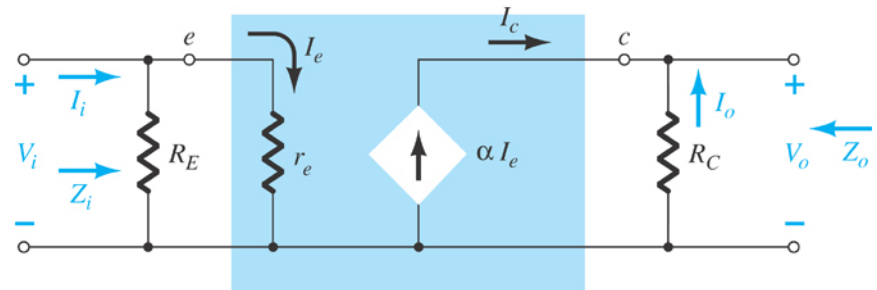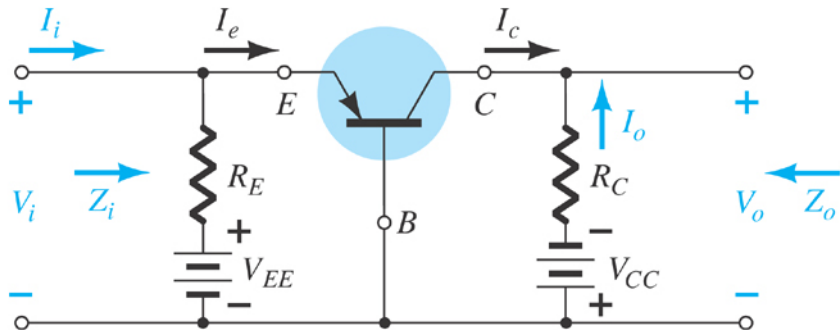




EEC2146: Electronic Circuits and Measurements

BJT Transistors

AC Analysis: **Common Base**

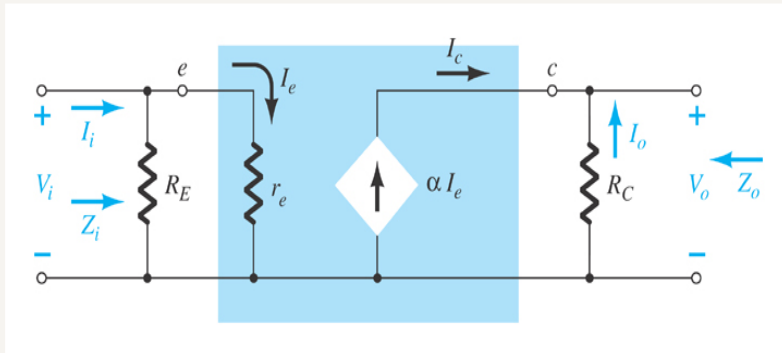

$$Z_i = R_E \parallel r_e$$

$$Z_o = R_C$$

$$A_v = \frac{V_o}{V_i} = \frac{\alpha R_C}{r_e} \cong \frac{R_C}{r_e}$$

$$A_i = \frac{I_o}{I_i} = -\alpha \cong -1$$



EEC2146: Electronic Circuits and Measurements



Questions